

## AC CIRCUITS

We would like to analyze the voltage-current relations for individual circuit elements carrying an AC-current.

### 33.2 Resistors in an AC Circuit

Consider a simple AC circuit consisting of a resistor and an AC source as shown in Figure 33.2. At any instant, the algebraic sum of the voltages around a closed loop in a circuit must be zero (Kirchhoff's loop rule). Therefore,  $\Delta v + \Delta v_R = 0$  or, using Equation 27.7 for the voltage across the resistor,

$$\Delta v - i_R R = 0$$

If we rearrange this expression and substitute  $\Delta V_{\max} \sin \omega t$  for  $\Delta v$ , the instantaneous current in the resistor is


$$i_R = \frac{\Delta v}{R} = \frac{\Delta V_{\max}}{R} \sin \omega t = I_{\max} \sin \omega t \quad (33.1)$$

where  $I_{\max}$  is the maximum current:

$$I_{\max} = \frac{\Delta V_{\max}}{R} \quad (33.2)$$

Equation 33.1 shows that the instantaneous voltage across the resistor is

$$\Delta v_R = i_R R = I_{\max} R \sin \omega t \quad (33.3)$$

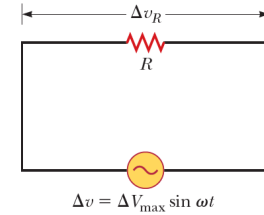


**Figure 33.2** A circuit consisting of a resistor of resistance  $R$  connected to an AC source, designated by the symbol

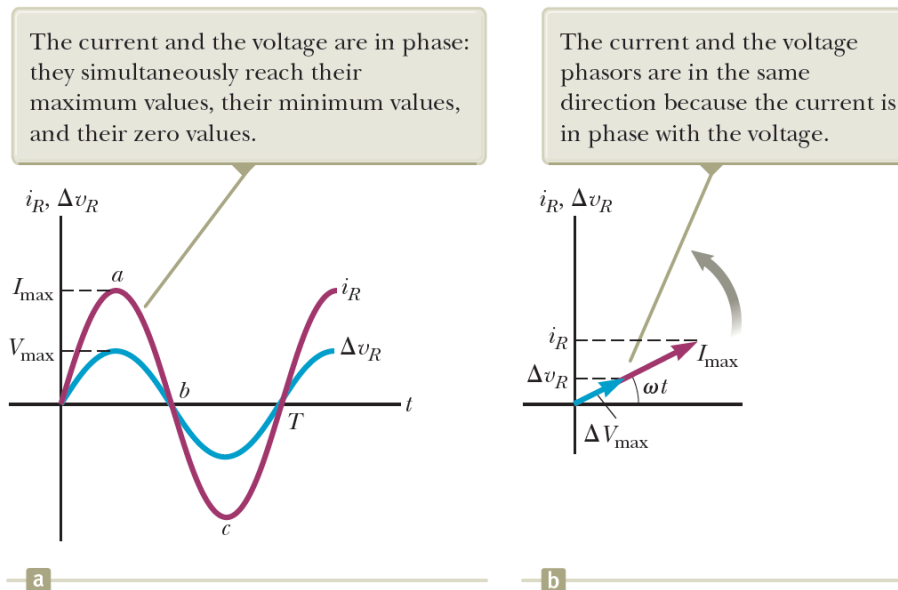


◀ Maximum current in a resistor

◀ Voltage across a resistor



**Since  $I_R$  and  $V_R$  both vary as  $\sin(\omega t)$  and they reach their maximum values at the same time, we say that the current and voltage across a resistor are in phase.**

Resistors behave the same in AC and DC circuits. However, capacitors and inductors don't!

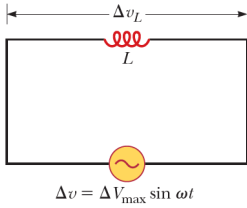

**Figure 33.6** A circuit consisting of an inductor of inductance  $L$  connected to an AC source.

### 33.3 Inductors in an AC Circuit

Now consider an AC circuit consisting only of an inductor connected to the terminals of an AC source as shown in Figure 33.6. Because  $\Delta v_L = -L(di_L/dt)$  is the self-induced instantaneous voltage across the inductor (see Eq. 32.1), Kirchhoff's loop rule applied to this circuit gives  $\Delta v + \Delta v_L = 0$ , or

$$\Delta v - L \frac{di_L}{dt} = 0$$

Substituting  $\Delta V_{\max} \sin \omega t$  for  $\Delta v$  and rearranging gives

$$\Delta v = L \frac{di_L}{dt} = \Delta V_{\max} \sin \omega t \quad (33.6)$$

Solving this equation for  $di_L$  gives

$$di_L = \frac{\Delta V_{\max}}{L} \sin \omega t dt$$

Integrating this expression<sup>1</sup> gives the instantaneous current  $i_L$  in the inductor as a function of time:

$$i_L = \frac{\Delta V_{\max}}{L} \int \sin \omega t dt = -\frac{\Delta V_{\max}}{\omega L} \cos \omega t \quad (33.7)$$


Using the trigonometric identity  $\cos \omega t = -\sin(\omega t - \pi/2)$ , we can express Equation 33.7 as

$$i_L = \frac{\Delta V_{\max}}{\omega L} \sin \left( \omega t - \frac{\pi}{2} \right) \quad (33.8)$$

Current in an inductor ►

Comparing this result with Equation 33.6 shows that the instantaneous current  $i_L$  in the inductor and the instantaneous voltage  $\Delta v_L$  across the inductor are *out of phase* by  $\pi/2$  rad =  $90^\circ$ .

▶▶▶ IIII

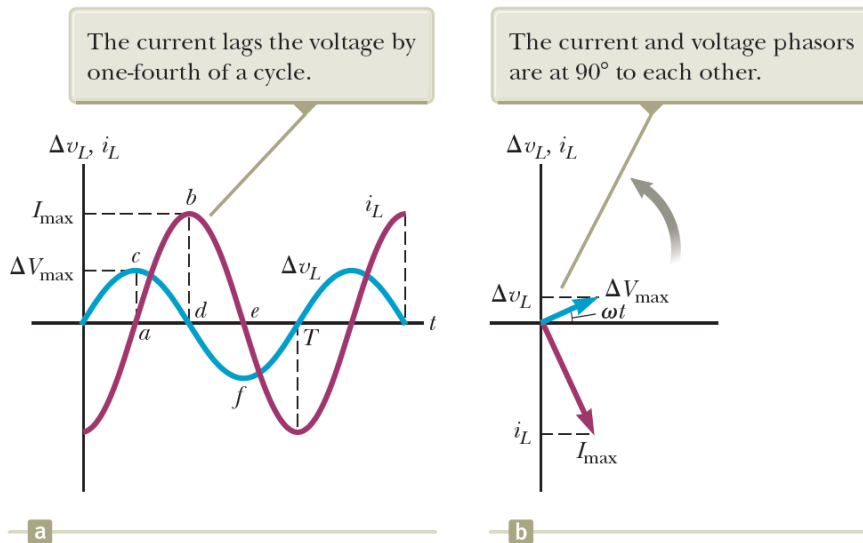

**For an AC applied voltage, the current in an inductor always lags behind the voltage across the inductor by  $90^\circ$ .**

Equation 33.7 shows that the current in an inductive circuit reaches its maximum value when  $\cos \omega t = \pm 1$ :

$$I_{\max} = \frac{\Delta V_{\max}}{\omega L} \quad (33.9)$$

$$X_L \equiv \omega L \quad (33.10) \quad \leftarrow \text{Inductive reactance}$$

Therefore, we can write Equation 33.9 as

$$I_{\max} = \frac{\Delta V_{\max}}{X_L} \quad (33.11)$$


Using Equations 33.6 and 33.11, we find that the instantaneous voltage across the inductor is

Voltage across an inductor  $\blacktriangleright$  
$$\Delta v_L = -L \frac{di_L}{dt} = -\Delta V_{\max} \sin \omega t = -I_{\max} X_L \sin \omega t \quad (33.12)$$

## 33.4 Capacitors in an AC Circuit

Figure 33.9 shows an AC circuit consisting of a capacitor connected across the terminals of an AC source. Kirchhoff's loop rule applied to this circuit gives  $\Delta v + \Delta v_C = 0$ , or

$$\Delta v - \frac{q}{C} = 0 \quad (33.13)$$

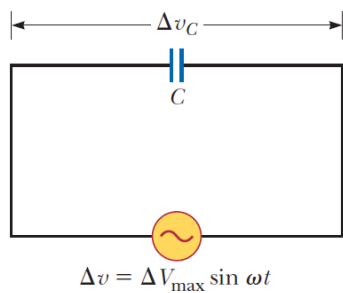

**Figure 33.9** A circuit consisting of a capacitor of capacitance  $C$  connected to an AC source.

Substituting  $\Delta V_{\max} \sin \omega t$  for  $\Delta v$  and rearranging gives

$$q = C \Delta V_{\max} \sin \omega t \quad (33.14)$$

where  $q$  is the instantaneous charge on the capacitor. Differentiating Equation 33.14 with respect to time gives the instantaneous current in the circuit:

$$i_C = \frac{dq}{dt} = \omega C \Delta V_{\max} \cos \omega t \quad (33.15)$$


Using the trigonometric identity

$$\cos \omega t = \sin \left( \omega t + \frac{\pi}{2} \right)$$

we can express Equation 33.15 in the alternative form

$$i_C = \omega C \Delta V_{\max} \sin \left( \omega t + \frac{\pi}{2} \right) \quad (33.16) \quad \blacktriangleleft$$

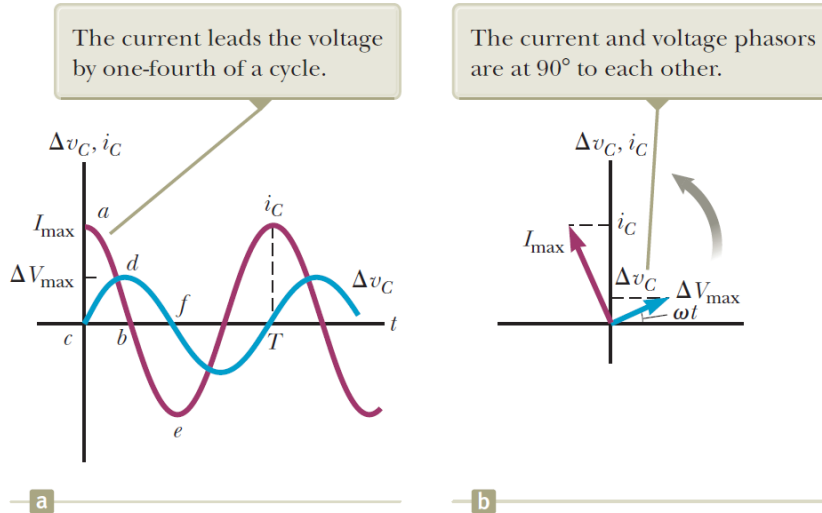Comparing this expression with  $\Delta v = \Delta V_{\max} \sin \omega t$  shows that the current is  $\pi/2$  rad =  $90^\circ$  out of phase with the voltage across the capacitor. A plot of current and voltage versus time (Fig. 33.10a) shows that the current reaches its maximum value one-quarter of a cycle sooner than the voltage reaches its maximum value.



**For an AC applied voltage, the current always leads the voltage across a capacitor by  $90^\circ$ .**

Equation 33.15 shows that the current in the circuit reaches its maximum value when  $\cos \omega t = \pm 1$ :

$$I_{\max} = \omega C \Delta V_{\max} = \frac{\Delta V_{\max}}{(1/\omega C)} \quad (33.17)$$

As in the case with inductors, this looks like Equation 27.7, so the denominator plays the role of resistance, with units of ohms. We give the combination  $1/\omega C$  the symbol  $X_C$ , and because this function varies with frequency, we define it as the **capacitive reactance**:

▶ 
$$X_C \equiv \frac{1}{\omega C} \quad (33.18)$$

We can now write Equation 33.17 as

▶ 
$$I_{\max} = \frac{\Delta V_{\max}}{X_C} \quad (33.19)$$

The rms current is given by an expression similar to Equation 33.19, with  $I_{\max}$  replaced by  $I_{\text{rms}}$  and  $\Delta V_{\max}$  replaced by  $\Delta V_{\text{rms}}$ .

Using Equation 33.19, we can express the instantaneous voltage across the capacitor as

▶ 
$$\Delta v_C = \Delta V_{\max} \sin \omega t = I_{\max} X_C \sin \omega t \quad (33.20)$$